

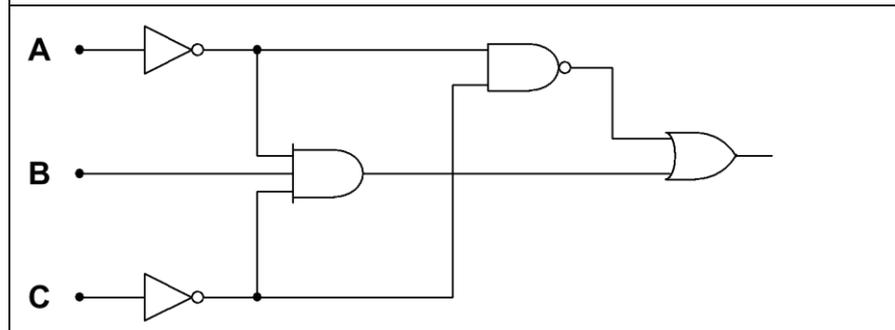
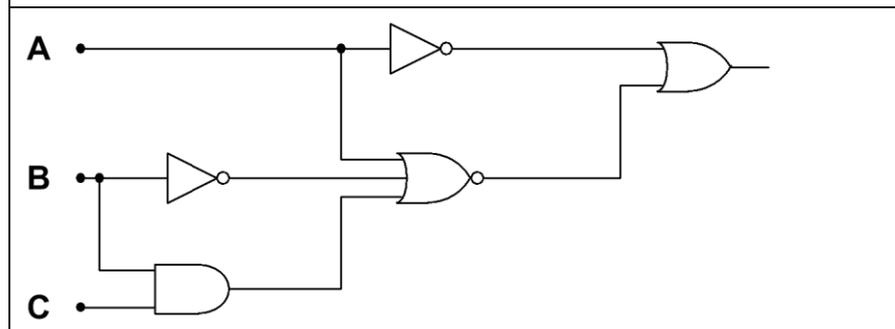
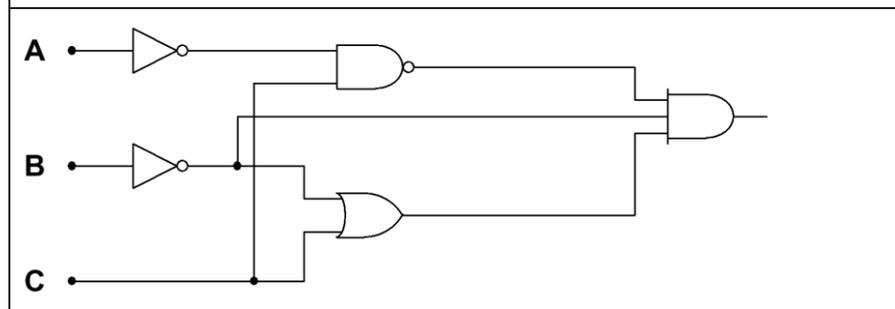
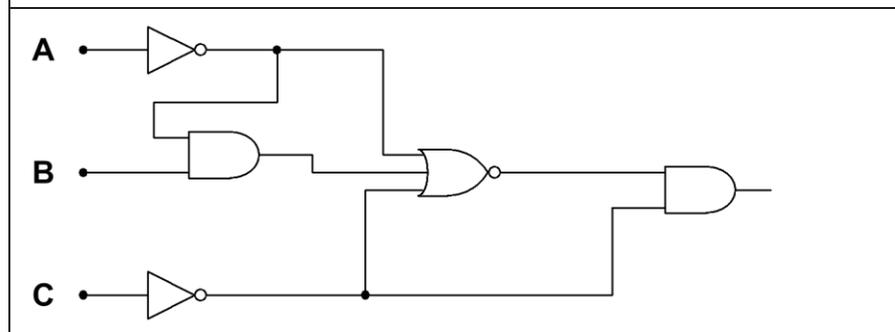
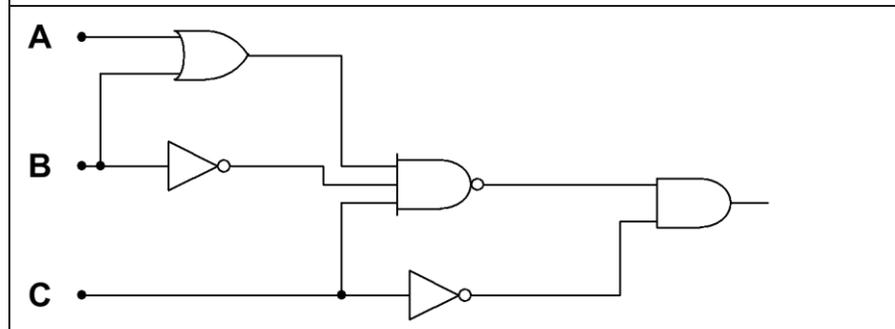


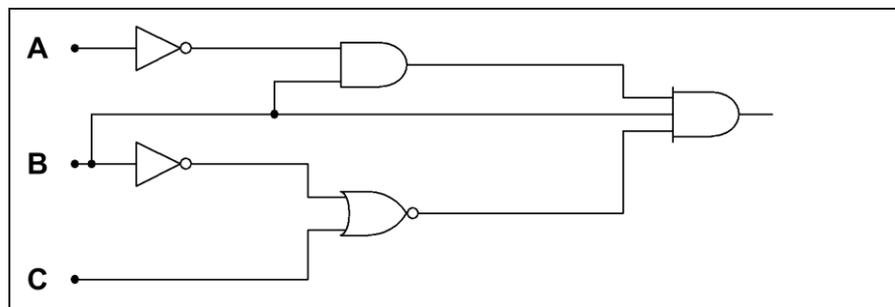STA - ESERCIZI SULL'ANALISI DEI CIRCUITI COMBINATORI



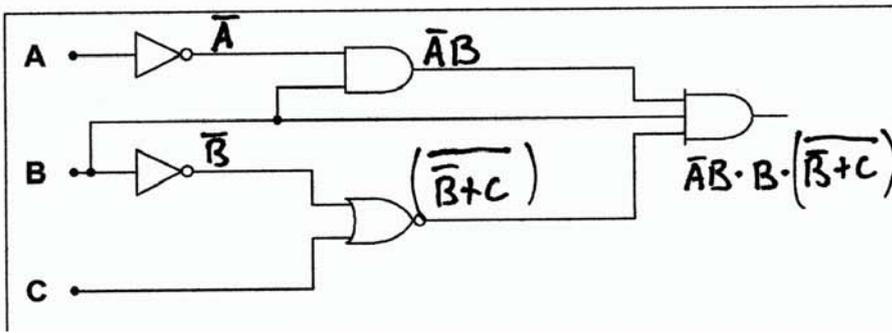

ABC	\bar{A}	\bar{B}	$\bar{A}B$	$\bar{B}+C$	$\overline{\bar{B}+C}$	U
000	1	1	0	1	0	0
001	1	1	0	1	0	0
010	1	0	1	0	1	1
011	1	0	1	1	0	0
100	0	1	0	1	0	0
101	0	1	0	1	0	0
110	0	0	0	0	1	0
111	0	0	0	1	0	0